

## Resistance

---

(i) The property of substance by virtue of which it opposes the flow of current through it, is known as the resistance.

(ii) **Formula of resistance** : For a conductor if  $l$  = length of a conductor  $A$  = Area of cross-section of conductor,  $n$  = No. of free electrons per unit volume in conductor,  $\tau$  = relaxation time then resistance of conductor  $R = \rho \frac{l}{A} = \frac{m}{ne^2 \tau} \cdot \frac{l}{A}$  ; where  $\rho$  = resistivity of the material of conductor

(iii) **Unit** : It's S.I. unit is *Volt/Amp.* or *Ohm* ( $\Omega$ ). Also 1 *ohm*  
$$= \frac{1 \text{ volt}}{1 \text{ Amp}} = \frac{10^8 \text{ emu of potential}}{10^{-1} \text{ emu of current}} = 10^9 \text{ emu of resistance}$$

(iv) **Dependence of resistance** : Resistance of a conductor depends upon the following factors.

(a) **Length of the conductor** : Resistance of a conductor is directly proportional to it's length *i.e.*  $R \propto l$  and inversely proportional to it's area of cross-section *i.e.*  $R \propto \frac{1}{A}$

(b) **Temperature** : For a conductor

**Resistance  $\propto$  temperature .**

If  $R_0$  = resistance of conductor at  $0^\circ\text{C}$

$R_t$  = resistance of conductor at  $t^\circ\text{C}$

and  $\alpha$  = temperature co-efficient of resistance

then  $R_t = R_0(1 + \alpha t)$  for  $t \leq 300^\circ\text{C}$  or  $\alpha = \frac{R_t - R_0}{R_0 \times t}$


If  $R_1$  and  $R_2$  are the resistances at  $t_1^\circ\text{C}$  and  $t_2^\circ\text{C}$  respectively then  $\frac{R_1}{R_2} = \frac{1 + \alpha t_1}{1 + \alpha t_2}$ .

The value of  $\alpha$  is different at different temperature. Temperature coefficient of resistance averaged over the temperature range  $t_1^\circ\text{C}$  to  $t_2^\circ\text{C}$  is given by  $\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)}$  which gives  $R_2 = R_1 [1 + \alpha (t_2 - t_1)]$ . This formula gives an approximate value.

## Combination of Resistors

### (1) Series Combination

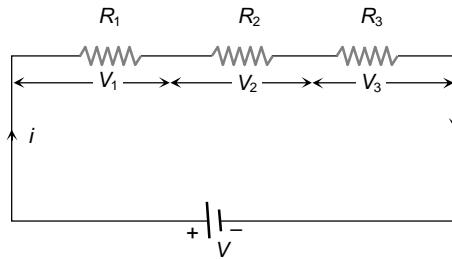(i) Same current flows through each resistance but potential difference distributes in the ratio of resistance *i.e.*  $V \propto R$



(ii)  $R_{eq} = R_1 + R_2 + R_3$  equivalent resistance is greater than the maximum value of resistance in the combination.


(iii) If  $n$  identical resistance are connected in series  $R_{eq} = nR$  and potential difference across each resistance  $V' = \frac{V}{n}$

### (2) Parallel Combination

(i) Same potential difference appeared across each resistance but current distributes in the reverse ratio of their resistance *i.e.*  $i \propto \frac{1}{R}$

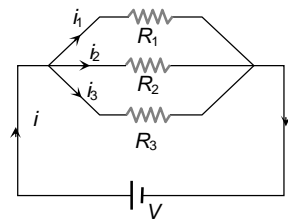(ii) Equivalent resistance is given by  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$  or

$$R_{eq} = (R_1^{-1} + R_2^{-1} + R_3^{-1})^{-1} \text{ or } R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$



Equivalent resistance is smaller than the minimum value of resistance in the combination.


(iv) If two resistance in parallel  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{\text{Multiplication}}{\text{Addition}}$

(v) Current through any resistance

$$i' = i \times \left[ \frac{\text{Resistance of opposite branch}}{\text{Total resistance}} \right]$$

Where  $i'$  = required current (branch current),

$i$  = main current

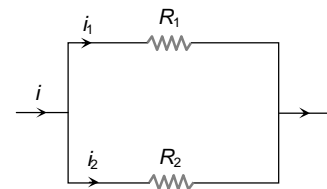

$$i_1 = i \left( \frac{R_2}{R_1 + R_2} \right) \text{ and } i_2 = i \left( \frac{R_1}{R_1 + R_2} \right)$$

(vi) In  $n$  identical resistance are connected in parallel

$$R_{eq} = \frac{R}{n} \text{ and current through each resistance } i' = \frac{i}{n}$$

### Electric cell :

- a) It is a device which converts chemical energy into electrical energy.
- b) There are two types of cells
  - i) Primary cell      ii) Secondary cell
- c) **comparison of primary and secondary cells:**

### Electromotive force (e.m.f) of a Cell :

- a) The work done in carrying a unit positive charge once in the whole circuit including the cell, is defined as the electromotive force.
- b) Electromotive force is the potential difference between the terminals of a cell in open circuit.
- c) Electromotive force depends on –(1) nature of electrolyte (2) metal of the electrodes.
- d) Electromotive force does not depend on (1) area of plates (2) distance between the electrodes (3) Quantity of electrolyte (4) size of the cell.
- e) Electromotive force is the characteristic property of the cell. The direction of current inside the cell is always from negative to positive electrode.
- f) The unit of electromotive force is volt.

### Internal resistance (r) :

The internal resistance of a cell is the resistance offered by the column of the electrolyte between the positive plate and the negative plate.

- i) The internal resistance of a perfect cell or ideal cell is zero.
- ii) Internal resistance depends on
  - a) strength of electrolyte ( $r \propto \text{strength}$ )
  - b) distance between plates ( $r \propto d$ )
  - c) area of the plates  $\left[ r \propto \frac{1}{A} \right]$
  - d) temperature of electrolyte  $\left[ r \propto \frac{1}{t} \right]$


## Relation between EMF and PD:

(i) In case of charging of a cell

a) The current flows from +ve to -ve terminal inside the cell.

b)  $V > E$

c)  $V = E + ir$

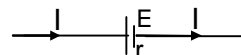


(ii) In case of discharge of a cell

a) The current flows from -ve to +ve terminal inside the cells

b)  $V < E$

c)  $V = E - ir$

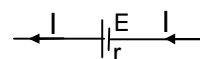

(iii) The difference between E and V is called **lost volts**


$$\therefore \text{lost volts} = E - V = ir$$

(iv) A cell of emf 'E' and its resistance 'r' is connected to resistance 'R'.

a)  $i = \frac{E}{R+r}$

b) P.D. across resistance R is given by

$$V = iR = \frac{ER}{R+r}$$

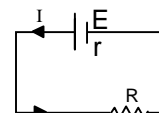

c) Fraction of energy useful  $= \frac{V}{E} = \frac{R}{R+r}$

d) % of fractional useful energy  $= \left(\frac{V}{E}\right)100 = \left(\frac{R}{R+r}\right)100$

e) Fraction of energy lost  $= \frac{E-V}{E} = \frac{ir}{E} = \frac{r}{R+r}$

f) % of lost energy  $= \left(\frac{r}{R+r}\right)100$

g)  $r = \frac{(E-V)R}{V}$

h) For single cell, the condition for maximum current is  $R = r$ .

## Back emf :

a) The copper electrode gets covered with a layer of hydrogen and this hinders flow of current. In the neighbourhood of both electrodes, the concentrations of ions get altered. This results in an emf acting in a direction opposite to the emf of the cell. This is called *back emf*.

b) This formation of hydrogen around the anode is called *polarization*.

c) To reduce the back e.m.f manganese dioxide and potassium dichromite are added to electrolyte of cell. These are called *depolarizers*.